

Translocator Switch Box Instructions

Version 2013November17

Copyright 2013 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com





This is an absolutely awesome switching device. Construction is very simple. This is a passive device, so there is no circuit board, just wire up the switch, jacks and LEDs.

Use the project documents provided, starting with the General Build Instructions. Wire the jacks, switch, resistor and LEDs according to the wiring diagram. Start by solder tacking the wiring to the LEDs and then wire the jacks and the switch.



Version 2013November17 Copyright 2013 JD Sleep Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

Here's an inside view of the unit we built to give you a real view of the construction.

