

Version 2006March31

Copyright 2006 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

This project is a hybrid of Scott Swartz's excellent PT-80 delay (Princeton Technologies PT2399 based - 300mS) and Dean Hazelwanter's previous HEcho delay based on the Holtek HT8955A (800mS). It came about due to requests to marry Scott's well thought out and designed project with a longer delay time. Please see Scott's detailed technical description of the PT-80 for design notes.

- Layout fits Hammond 1590C case.
- 1uF cap layout fits 1uF 63v box type metalized film caps. 1uF electrolytic can also be used; the + terminal pad is square, the terminal pad is round.
- Note that the value of R22 can be reduced from 150K to as low as 68K to reduce the minimum delay time available. Reducing R22 also lowers the maximum available delay time. If there is distortion and general mayhem with R22=68K and the delay pot turned down, increase R22 to 82K.
- C21 is mounted on the back of the PCB under U3. Care must be taken to avoid the cap leads from shorting to other traces. Electrical tape can be placed across the tracks for insulation before C21 is installed.
- Current draw is 27.5 mA.

Bill of Materials

Resistors	(1/4 watt	rating)
いてついしいつ	ı i/ + walı	i auiiu

1 - 4.7 ohm

3 - 1k

1 - 5k6 (5.6k)

12 - 10k

3 - 22k

2 - 36k

1-100k

1 - 150k

1 - 560k

2 - 1M

Pots (1/4 watt or higher rating)

2 - 50k linear

1 - 500k linear

ICs

1 – HT8955A

1 - 41256 (DRAM)

1 - SA571

1 - TL072

Capacitors (minimum 16 volt rating)

1 –47pF film or ceramic

2 –100pF film or ceramic

1 –470pF film or ceramic

1-0.001uF film

2 - 0.0022 uF film

1 - 0.01uF film

2-0.015uF film

1-0.033uF film

1 - 0.047 uF film

3 - 0.1uF film

2-0.47uF film

10–1uF aluminum electrolytic or film

4 – 100uF aluminum electrolytic



Version 2006March31

Copyright 2006 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

Other Parts

1-78L05 - 5 volt regulator

1 - 3PDT or DPDT heavy duty foot switch (bypass)

1 – mono quarter inch jack

1 – stereo quarter inch jack


9v battery snaps & holder and/or DC jack knobs, Copper-clad board, etchant, or perfboard

24 gauge stranded wire

Enclosure

Parts ordered by Name

R1 - 1k	R18 - 1k	C7 - 1uF	C24 - 100uF
R2 - 1M	R19 - 1M	C8 - 1uF	C25 - 100uF
R3 - 10k	R20 - 10k	C9 - 1uF	C26 - 0.1uF
R4 - 22k	R21 - 22k	C10 - 0.0022uF	C27 - 100uF
R5 - 36k	R22 - 150k	C11 - 0.033uF	C28 - 100uF
R6 - 36k	R23 - 5k6 (5.6k)	C12 - 0.001uF	C29 - 0.01uF
R7 - 22k	R24 - 5600k	C13 - 1uF	C30 - 1uF
R8 - 100k	R25 - 10k	C14 - 0.47uF	C31 - 1uF
R9 - 10k	R26 - 10k	C15 - 100pF	
R10 - 10k	R27 - 4.7 ohm	C16 - 1uF	U1 - TL072
R11 - 10k		C17 - 1uF	U2 - SA571N
R12 - 10k	C1 - 0.015uF	C18 - 0.015uF	U3 - 41256 DRAM
R13 - 10k	C2 - 0.047uF	C19 - 47pF	U4 - HT8955A
R14 - 10k	C3 - 470pF	C20 - 1uF	U5 - 78L05
R15 - 10k	C4 - 1uF	C21 - 0.1uF	
R16 - 10k	C5 - 0.47uF	C22 - 0.1uF	Q1 - 2N5088
R17 - 1k	C6 - 100pF	C23 - 0.0022uF	

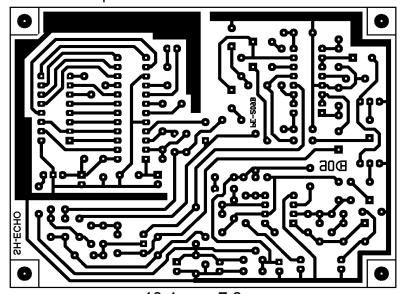


10.4cm x 7.8cm



Version 2006March31

Copyright 2006 JD Sleep

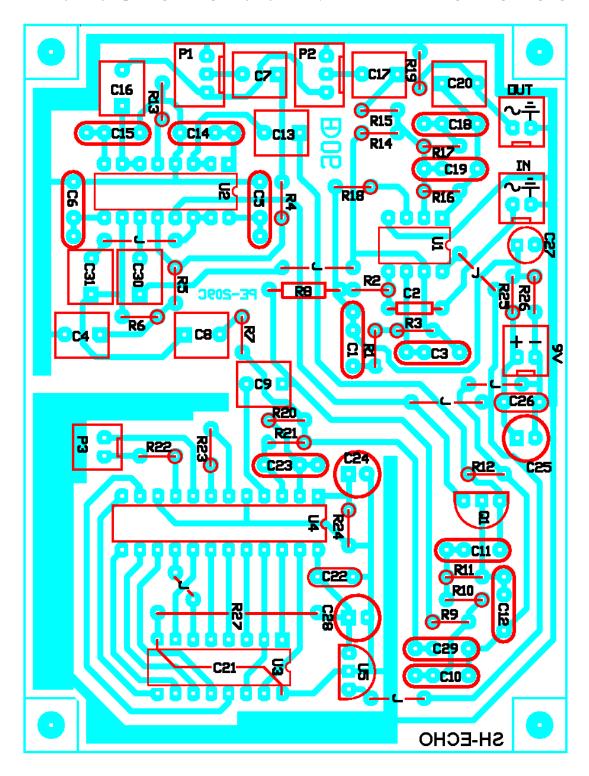Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com





Version 2006March31 Copyright 2006 JD Sleep Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

