PROJECT NAME

ACHILLES



BASED ON Analogman Prince of Tone


EFFECT TYPEAmp-like overdrive

BUILD DIFFICULTY■■□□□□ Easy

DOCUMENT VERSION 1.1.1 (2024-08-08)

PROJECT SUMMARY

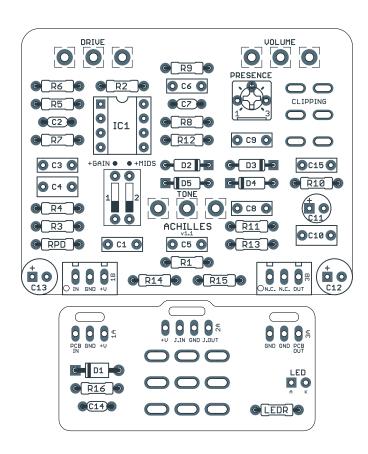A single-channel adaptation of the legendary King of Tone, with a few added features not found in the original dual-channel pedal.



Actual size is 2.3" x 1.86" (main board) and 1.78" x 0.87" (bypass board).

IMPORTANT NOTE —

This documentation is for the **PCB-only** version of the project. If you are building the full kit from Aion FX, please use the <u>kit build documentation</u> instead. The instructions are more detailed and may differ in some areas due to the specialized parts and assembly methods used in our kits.

TABLE OF CONTENTS

- 1 Project Overview
- 2 Introduction & Usage
- 3-5 Parts List
 - 6 Build Notes
 - 7 Schematic

- 8 Drill Template
- 9 Enclosure Layout
- 10 Wiring Diagram
- 11 Licensing
- **11** Document Revisions

INTRODUCTION

The Achilles Amp Overdrive is based on the Analogman Prince of Tone, the single-channel adaptation of the King of Tone that was first released in 2012. Unlike the King of Tone, the Prince was designed for mass production and is assembled in China. As a result, it's much more affordable as well as being readily available (the King of Tone has a 4 ½-year waiting list).

The Prince of Tone converts the internal diode DIP switch into an external toggle switch, allowing for soft clipping, hard clipping or no clipping to be selected without needing to open up the back. It also has the high gain mod from the King of Tone as standard.

Internally, in addition to the Presence control, there are two DIP switch settings that are new to this pedal. One of them adds low-mid frequencies to the first gain stage. The other is called "Turbo" mode that essentially doubles the gain of the second stage, meaning it reaches the clipping threshold sooner and has more apparent drive on tap.

The Achilles is a direct clone of the Prince of Tone with no modifications.

USAGE

The Achilles has four external controls:

- **Drive** controls the amount of gain going into the op-amp feedback diode clipping stage.
- **Tone** controls the treble response via a passive filter.
- **Volume** controls the overall output.
- **Clipping** (toggle switch) selects between soft clipping (overdrive), hard clipping (distortion) and no clipping (clean boost).

There are also three internal controls:

- **Presence** (trimmer) is an additional passive treble control. The default position is all the way down (full CCW) and as you turn it up it adds high-end. Noise or hiss will increase as well.
- +Mids (DIP switch) adds low-mids to the signal by increasing the filter frequency of the first op-amp gain stage.
- +Gain (DIP switch) doubles the gain ratio of the second op-amp stage so that the diodes clip more easily.

PARTS LIST

This parts list is also available in a spreadsheet format which can be imported directly into Mouser for easy parts ordering. Mouser doesn't carry all the parts—notably potentiometers—so the second tab lists all the non-Mouser parts as well as sources for each.

<u>View parts list spreadsheet</u> →

| PART | VALUE | ТҮРЕ | NOTES |
|--------------|------------|-------------------------------|---|
| R1 | 1M | Metal film resistor, 1/4W | |
| R2 | 10k | Metal film resistor, 1/4W | |
| R3 | 27k | Metal film resistor, 1/4W | |
| R4 | 33k | Metal film resistor, 1/4W | |
| R5 | 100k | Metal film resistor, 1/4W | |
| R6 | 10k | Metal film resistor, 1/4W | |
| R7 | 10k | Metal film resistor, 1/4W | |
| R8 | 220k | Metal film resistor, 1/4W | |
| R9 | 6k8 | Metal film resistor, 1/4W | |
| R10 | 1k | Metal film resistor, 1/4W | |
| R11 | 1k | Metal film resistor, 1/4W | |
| R12 | 6k8 | Metal film resistor, 1/4W | |
| R13 | 1M | Metal film resistor, 1/4W | |
| R14 | 47k | Metal film resistor, 1/4W | |
| R15 | 47k | Metal film resistor, 1/4W | |
| R16 | 100R | Metal film resistor, 1/4W | Power supply filter resistor. |
| RPD | 1M | Metal film resistor, 1/4W | Input pull-down resistor. |
| LEDR | 10k | Metal film resistor, 1/4W | LED current-limiting resistor. Adjust value to change LED brightness. |
| C1 | 22n | Film capacitor, 7.2 x 2.5mm | 10n in some units. |
| C2 | 100pF | MLCC capacitor, NP0/C0G | 750pF in some units. |
| C3 | 10n | Film capacitor, 7.2 x 2.5mm | |
| C4 | 1uF | Film capacitor, 7.2 x 3.5mm | |
| C5 | 10n | Film capacitor, 7.2 x 2.5mm | |
| C6 | 100n | Film capacitor, 7.2 x 2.5mm | |
| C7 | 47pF | MLCC capacitor, NP0/C0G | Not in original pedal, but recommended to prevent high-end oscillation. |
| C8 | 10n | Film capacitor, 7.2 x 2.5mm | |
| C9 | 10n | Film capacitor, 7.2 x 2.5mm | |
| C10 | 1uF | Film capacitor, 7.2 x 3.5mm | |
| C11 | 1uF | Electrolytic capacitor, 4mm | |
| C12 | 100uF | Electrolytic capacitor, 6.3mm | Reference voltage filter capacitor. |
| C13 | 100uF | Electrolytic capacitor, 6.3mm | Power supply filter capacitors. |
| C14 | 100n | MLCC capacitor, X7R | Power supply filter capacitors. |
| ЛСШПТ | EC AMD OVE | DDDIVE | 1 |

PARTS LIST, CONT.

| PART | VALUE | ТҮРЕ | NOTES |
|-------|----------------|--------------------------------|---|
| D1 | 1N5817 | Schottky diode, DO-41 | |
| D2 | BAS33 | Switching diode, DO-35 | Original uses MA856 diodes. The BAS33 is the closest available diode currently in production. |
| D3 | BAS33 | Switching diode, DO-35 | |
| D4 | BAS33 | Switching diode, DO-35 | |
| D5 | BAS33 | Switching diode, DO-35 | |
| IC1 | JRC4580D | Operational amplifier, DIP8 | |
| IC1-S | DIP-8 socket | IC socket, DIP-8 | |
| MODE | 2-pos. DIP | DIP switch, 2-position | |
| PRES. | 50k trimmer | Trimmer, 10%, 1/4" | |
| DRIVE | 100kB | 16mm right-angle PCB mount pot | |
| TONE | 25kB | 16mm right-angle PCB mount pot | |
| VOL. | 100kA | 16mm right-angle PCB mount pot | |
| CLIP | DPDT cntr. off | Toggle switch, DPDT on-off-on | |
| LED | 5mm | LED, 5mm, red diffused | |
| IN | 1/4" stereo | 1/4" phone jack, closed frame | Switchcraft 112BX or equivalent. |
| OUT | 1/4" mono | 1/4" phone jack, closed frame | Switchcraft 111X or equivalent. |
| DC | 2.1mm | DC jack, 2.1mm panel mount | Mouser 163-4302-E or equivalent. |
| FSW | 3PDT | Stomp switch, 3PDT | |
| ENC | 125B | Enclosure, die-cast aluminum | Can also use a Hammond 1590N1. |

BUILD NOTES

Clipping diodes

The Prince of Tone uses MA856 diodes, which clip at a slightly higher threshold than standard silicon diodes such as 1N914 (approximately 0.82V compared to 0.7V). These diodes are long out of production and have almost entirely disappeared from the old-stock market, likely all bought up by Analogman and other cloners.

The BA282 and BA283 are very close to the MA856, and were the popular substitute among builders for awhile... until they dried up too.

Now, the closest option is the BAS33. These clip at around 0.8V, still significantly higher than the 1N914 and only slightly lower than the MA856. We've compared the curves on a Peak DCA75 and confirmed that they closely match the MA856 across the current test range.


The only problem is that the BAS33 went end-of-life in early 2022. Availability is still high, but eventually they'll join the ranks of the others.

Clipping switch

The DPDT on-off-on switch allows for three settings: soft clipping (diodes in op-amp feedback loop), hard clipping (diodes to ground after the second op-amp stage) or no clipping (all diodes lifted). If you do not need the middle clean boost setting, you can instead use a DPDT on-on switch.

However, note that since the diodes are shared between the two settings and "relocated" in each position, you cannot use an on-on-on switch to use both sets of diodes at the same time or it will cause issues with the circuit.

v1.1 update: Clipping switch wiring has been updated based on review of original trace. C15 and R10 are shorted (removed from the circuit) when in soft-clipping mode and the signal only passes through them in hard-clipping mode. It makes no sonic difference whether these are in or out of the circuit since there is no frequency-shaping. However, we strive for electronic accuracy in everything and not just tonal accuracy, so we've updated the PCB to match the original.

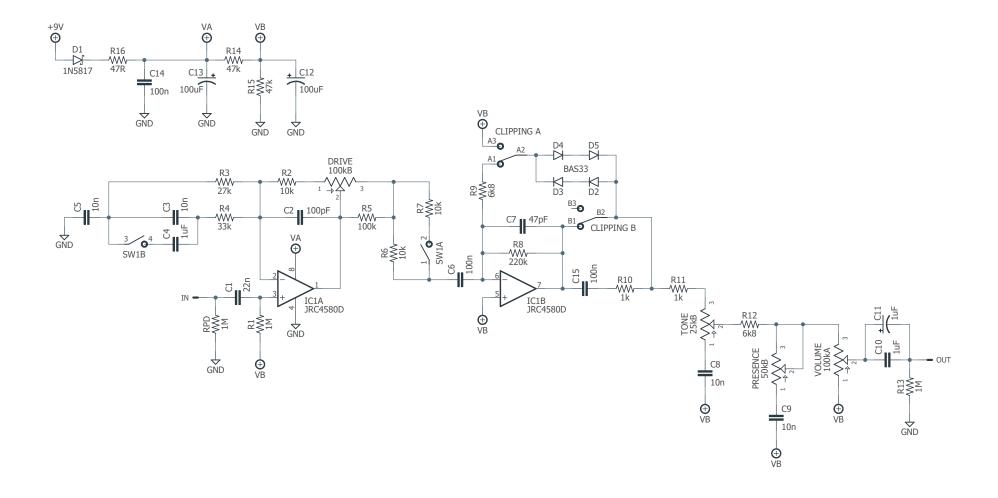


DRILL TEMPLATE

Cut out this drill template, fold the edges and tape it to the enclosure. Before drilling, it's recommended to first use a center punch for each of the holes to help guide the drill bit.

Ensure that this template is printed at 100% or "Actual Size". You can double-check this by measuring the scale on the printed page.


Top jack layout assumes the use of closed-frame jacks like the <u>Switchcraft 111X</u>. If you'd rather use open-frame jacks, please refer to the <u>Open-Frame Jack Drill Template</u> for the top side.

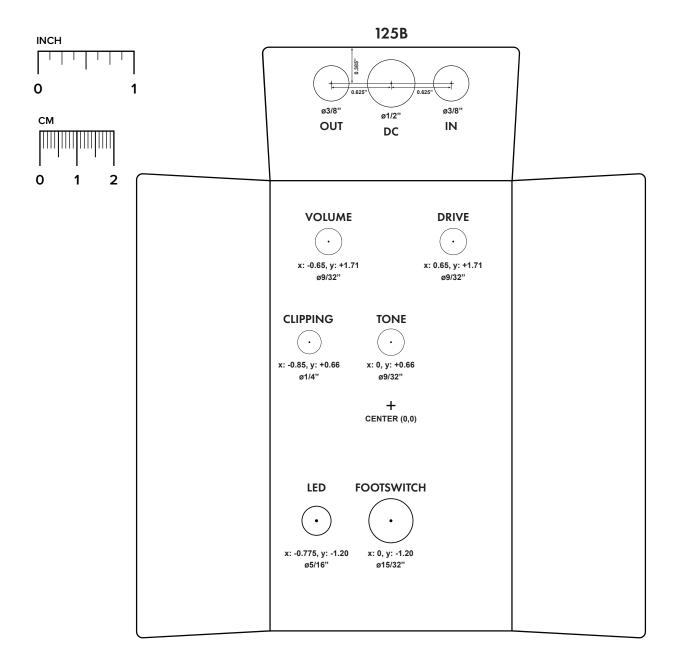
LED hole drill size assumes the use of a <u>5mm LED bezel</u>, available from several parts suppliers. Adjust size accordingly if using something different, such as a 3mm bezel, a plastic bezel, or just a plain LED.



ENCLOSURE LAYOUT

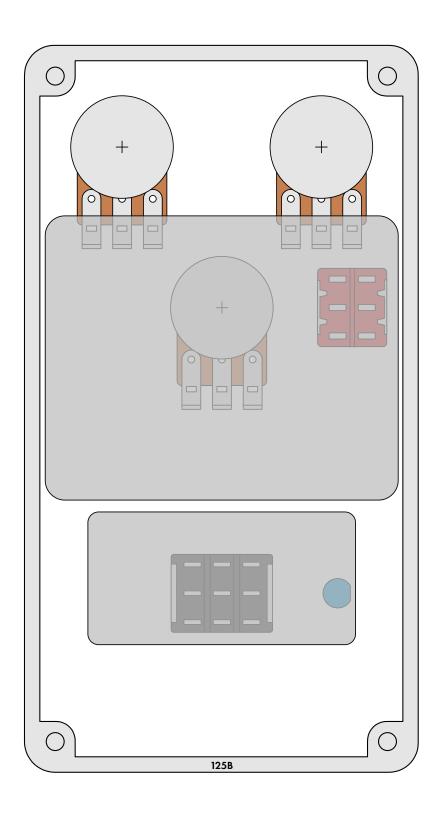Enclosure is shown without jacks. See next page for jack layout and wiring.



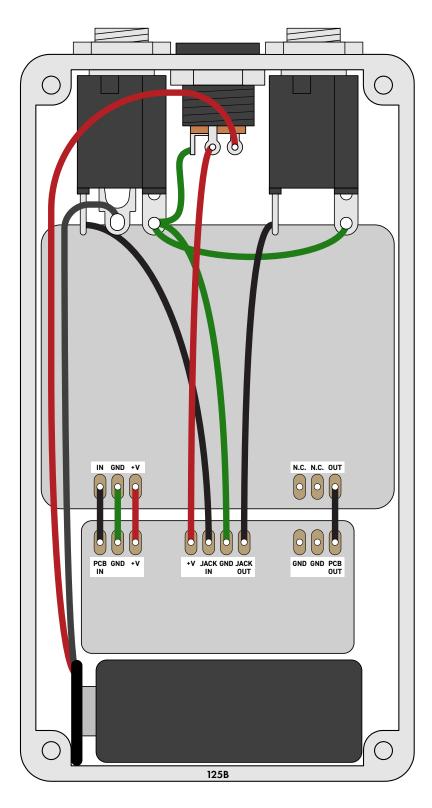

Shown with optional 9V battery. If battery is omitted, both jacks can be mono rather than one being stereo. Leave the far-right lug of the DC jack unconnected.

LICENSE & USAGE

No direct support is offered for these projects beyond the provided documentation. It's assumed that you have at least some experience building pedals before starting one of these. Replacements and refunds cannot be offered unless it can be shown that the circuit or documentation are in error.

All of these circuits have been tested in good faith in their base configurations. However, not all the modifications or variations have necessarily been tested. These are offered only as suggestions based on the experience and opinions of others.

Projects may be used for commercial endeavors in any quantity unless specifically noted. No attribution is necessary, though a link back is always greatly appreciated. The only usage restrictions are that (1) you cannot resell the PCB as part of a kit without prior arrangement, and (2) you cannot "goop" the circuit, scratch off the screenprint, or otherwise obfuscate the circuit to disguise its source. (In other words: you don't have to go out of your way to advertise the fact that you use these PCBs, but please don't go out of your way to hide it. The guitar effects industry needs more transparency, not less!)

DOCUMENT REVISIONS

1.1.1 (2024-08-08)

Changed LEDR to 10k to work with a wider variety of LEDs.

1.1.0 (2023-05-15)

- Updated clipping switch configuration based on reviewing original trace. See page 5 for details.
- Changed R2 to 10k (mistakenly listed as 100k in schematic and parts list).

1.0.1 (2022-09-02)

Changed RPD value to 1M (shown as 2M2 in schematic and omitted from PDF parts list). The Mouser parts list was correct.

1.0.0 (2022-04-08)

Initial release.